

For battery detection and monitoring, R11, R12 and Q2 reduce the output voltage to approximately 8 V when a 5 V signal is applied to R12. This allows the battery voltage to be measured, giving the state of charge.

Key Design Points

- The value of R3 sets the typical output current limit threshold given by: $R3 = 0.6 / I_{LIMIT}$.
- Rate R3 and R5 accordingly for power dissipation (1 W).
- Ensure total voltage across R3 and R5 is greater than 1.5 V at I_{LIMIT} if control to 0 V (output shorted) is required.
- Ensure voltage at cathode of D3 is >6 V at I_{LIMIT} . Add additional bias winding turns, if necessary, to maintain output current control to 0 V (output shorted).
- RT1: Philips part # 2322-640-54472.
- Select tolerance of U2, R7, R8 and R9 to give the desired overall CV tolerance (R7, R8 and R9 as 0.1%; R10 as 1% and U2 as 0.5% gives overall tolerance <2%).

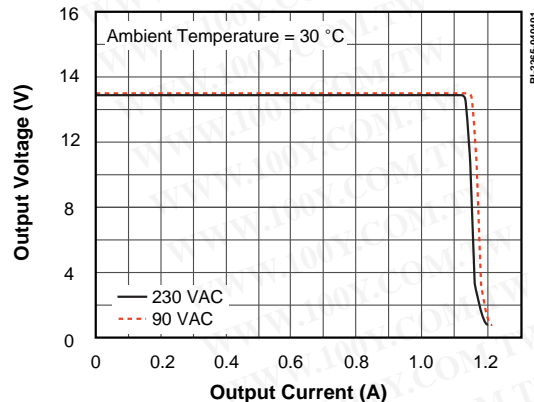


Figure 2. Output Characteristic (V_{OUT} vs I_{OUT})

TRANSFORMER PARAMETERS	
Core Material	TDK PC40 EE22/29/6-Z, Gap for $A_{LG} = 145 \text{ nH/T}^2$
Bobbin	YC 2204 (Ying Chin)
Winding Details	Primary: 56T, 30 AWG Bias: 8T, 2 x 30 AWG Secondary: 8T, 28 AWG T.I.W. (T.I.W. = Triple Insulated Wire)
Winding Order (Pin Numbers)	Primary (2-1), tape, Bias (4-3), tape, Secondary (7,8-5,6)
Inductance	Primary: 475 $\mu\text{H} \pm 10\%$, Leakage: 35 μH (maximum)
Primary Resonant Frequency	300 kHz (minimum)

Table 1. Transformer Construction Information.

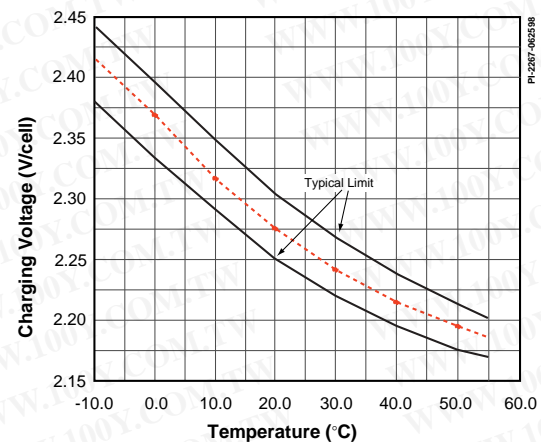


Figure 3. Cell Charging Voltage vs Temperature.

For the latest updates, visit our Web site: www.powerint.com

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability.

Power Integrations does not assume any liability arising from the use of any device or circuit described herein, nor does it convey any license under its patent rights or the rights of others. The products and applications illustrated herein (including circuits external to the products and transformer construction) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com.

The PI Logo, TOPSwitch, TinySwitch, LinkSwitch and EcoSmart are registered trademarks of Power Integrations, Inc. PI Expert is a trademark of Power Integrations, Inc. ©Copyright 2002, Power Integrations, Inc.

WORLD HEADQUARTERS AMERICAS

Power Integrations, Inc.
 San Jose, CA 95138 USA
 Customer Service:
 Phone: +1 408-414-9665
 Fax: +1 408-414-9765
 e-mail: usasales@powerint.com

CHINA

Power Integrations International
 Holdings, Inc.
 China
 Phone: +86-755-8367-5143
 Fax: +86-755-8377-9610
 e-mail: chinasales@powerint.com

EUROPE & AFRICA

Power Integrations (Europe) Ltd.
 United Kingdom
 Phone: +44-1344-462-300
 Fax: +44-1344-311-732
 e-mail: eurosales@powerint.com

KOREA

Power Integrations
 International Holdings, Inc.
 Seoul, Korea
 Phone: +82-2-782-2840
 Fax: +82-2-782-4427
 e-mail: koreasales@powerint.com

SINGAPORE

Power Integrations, Singapore
 Republic of Singapore 308900
 Phone: +65-6358-2160
 Fax: +65-6358-2015
 e-mail: singaporesales@powerint.com

JAPAN

Power Integrations, K.K.
 Keihin-Tatemono 1st Bldg.
 Japan
 Phone: +81-45-471-1021
 Fax: +81-45-471-3717
 e-mail: japansales@powerint.com

APPLICATIONS HOTLINE

World Wide +1-408-414-9660

TAIWAN

Power Integrations
 International Holdings, Inc.
 Taipei, Taiwan
 Phone: +886-2-2727-1221
 Fax: +886-2-2727-1223
 e-mail: taiwansales@powerint.com

INDIA (Technical Support)

Innovatech
 Bangalore, India
 Phone: +91-80-226-6023
 Fax: +91-80-228-9727
 e-mail: indiasales@powerint.com

APPLICATIONS FAX

World Wide +1-408-414-9760