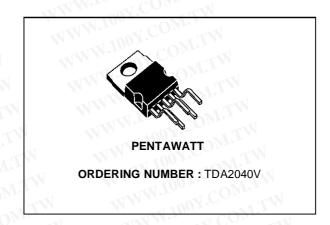



20W Hi-Fi AUDIO POWER AMPLIFIER

DESCRIPTION

The TDA2040 is a monolithic integrated circuit in Pentawatt ® package, intended for use as an audio class AB amplifier. Typically it provides 22W output power (d = 0.5%) at $V_{s}=32\text{V}/4\Omega$. The TDA2040 provides high output current and has very low harmonic and cross-over distortion. Further the device incorporates a patented short circuit protection system comprising an arrangement for automatically limiting the dissipated power so as to keep the working point of the output transistors within their safe operating area. A thermal shut-down system is also included.





TEST CIRCUIT

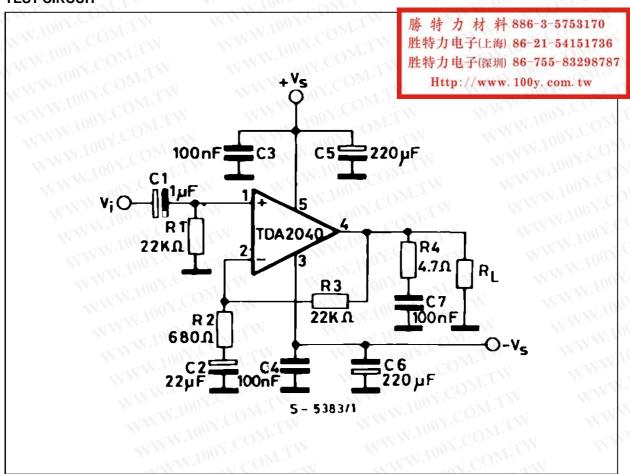

December 1995 1/13

SCHEMATIC DIAGRAM

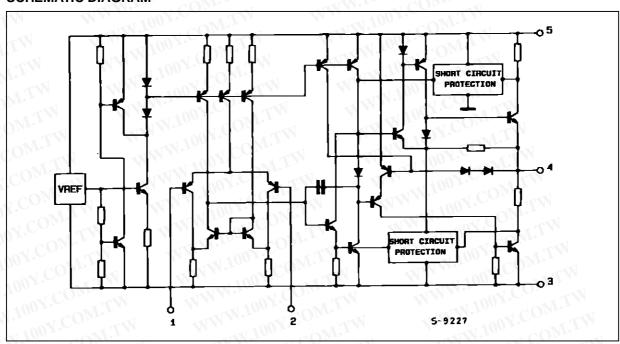

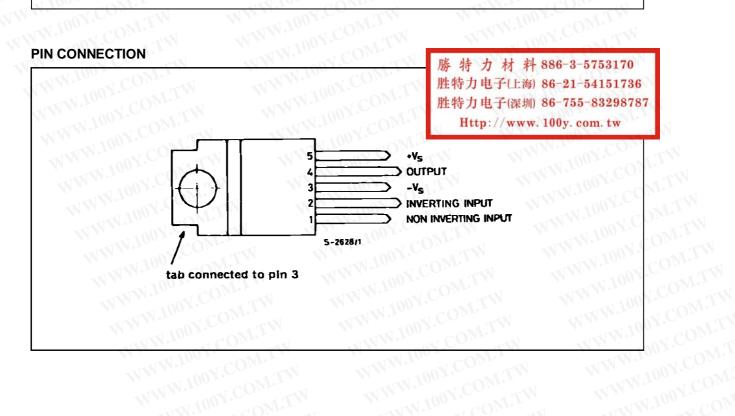

THERMAL DATA

IERMAL Symbol	DATA Parameter	MMM.1001	Value	Unit	
th j-case	Thermal Resistance Junction-case	Max.	3	°C/W	

ABSOLUTE MAXIMUM RATINGS

Symbol	Parameter	Value	Unit
Vs	Supply Voltage	± 20	V
Vi	Input Voltage	V _s	
Vi	Differential Input Voltage	± 15	V
lo	Output Peak Current (internally limited)	4	А
P _{tot}	Power Dissipation at T _{case} = 75 °C	25	W
T _{stg} , T _j	Storage and Junction Temperature	- 40 to + 150	°C

WWW.100Y.COM.T

ELECTRICAL CHARACTERISTICS (refer to the test circuit 1/2 (refer to the test circuit, $V_S = \pm 16V$, $T_{amb} = 25^{\circ}C$ unless otherwise specified)

Symbol	Parameter	Test Conditions	Min.	Тур.	Max.	Unit
Vs	Supply Voltage	M. T. M. T. M. T.	± 2.5		± 20	٧
l _d	Quiescent Drain Current	$V_{S} = \pm 4.5V$ $V_{S} = \pm 20V$	100 x	45	30 100	mA mA
10 l _b	Input Bias Current	$V_s = \pm 20V$	Tan	0.3	1	μΑ
Vos	Input Offset Voltage	$V_s = \pm 20V$	N.100	± 2	± 20	mV
l _{os}	Input Offset Current	CO. TW	110	01.0	± 200	nA
Po	Output Power	$\begin{array}{l} \text{d} = 0.5\%, T_{\text{case}} = 60^{\circ}\text{C} \\ \text{f} = 1\text{kHz} & \text{R}_{\text{L}} = 4\Omega \\ \text{R}_{\text{L}} = 8\Omega \\ \text{f} = 15\text{kHz} & \text{R}_{\text{L}} = 4\Omega \end{array}$	20 15	22 12 18	COM	W
BW	Power Bandwidth	$P_0 = 1W, R_L = 4\Omega$	11/11/11	100	V.Co	kHz
G _v	Open Loop Voltage Gain	f = 1kHz	NVV	80	V.C	dB
Gv	Closed Loop Voltage Gain	f = 1kHz	29.5	30	30.5	dB
d	Total Harmonic Distortion	$P_{o} = 0.1 \text{ to } 10W, R_{L} = 4\Omega$ f = 40 to 15000Hz f = 1kHz	M	0.08 0.03	100A.	%
en	Input Noise Voltage	B = Curve A B = 22Hz to 22kHz	V	2 3	10	μV μV
İN	Input Noise Current	B = Curve A B = 22Hz to 22kHz		50 80	200	pA
Ri	Input Resistance (pin 1)	1, 100 r. COM:11.	0.5	5	TN.1	МΩ
SVR	Supply Voltage Rejection	$\begin{aligned} R_L &= 4\Omega, R_g = 22k\Omega, G_v = 30dB \\ f &= 100Hz, V_{ripple} = 0.5V_{RMS} \end{aligned}$	40	50	WW.	dB
η	Efficiency	$ \begin{aligned} f &= 1 \text{kHz} \\ P_0 &= 12 \text{W} & \text{RL} = 8 \ \Omega \\ P_0 &= 22 \text{W} & \text{RL} = 4 \ \Omega \end{aligned} $	N	66 63	WW	%
Tj	Thermal Shut-down Junction Temperature	MALL		145	MAN	°C

WWW.100Y.COM.TW 勝 特 力 材 料 886-3-5753170 胜特力电子(上海) 86-21-54151736 胜特力电子(深圳) 86-755-83298787 Http://www. 100y. com. tw



WW.100Y.COM.TW

W.100Y.COM.TW

WWW.100Y.COM.T

Figure 1: Output Power versus Supply Voltage

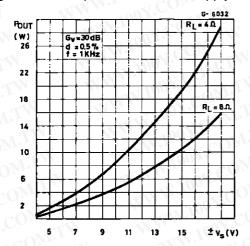


Figure 3: Output Power versus Supply Voltage

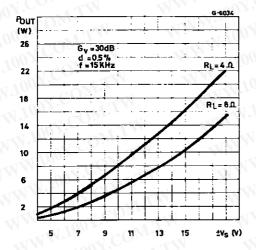


Figure 5 : Supply Voltage Rejection versus Frequency

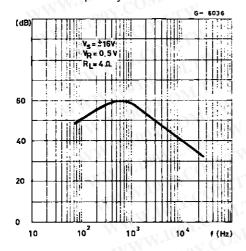


Figure 2: Output Power versus Supply Voltage

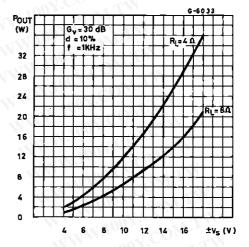


Figure 4: Distortion versus Frequency



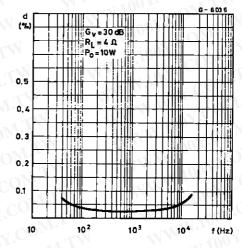



Figure 6 : Supply Voltage Rejection versus Voltage Gain

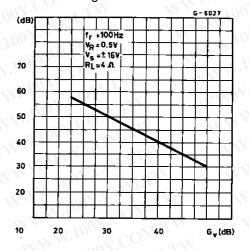

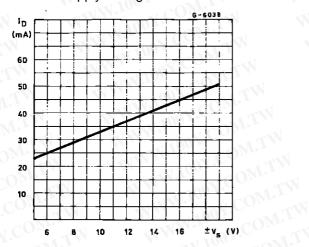Quiescent Drain Current versus Figure 7: Supply Voltage




Y.COM.TW Figure 9: Power Dissipation versus Output Power

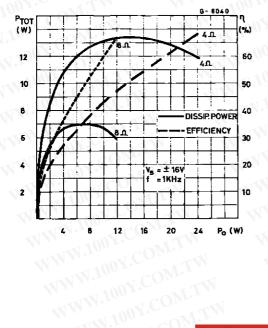

WWW.100Y.COM

WWW.100Y.C

Figure 8: Open Loop Gain versus Frequency

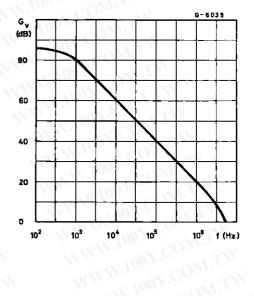

WWW.100Y.COM.TW 特力材料886-3-5753170 胜特力电子(上海) 86-21-54151736 胜特力电子(深圳) 86-755-83298787 Http://www. 100y. com. tw

WWW.100Y.COM.TW

WW.100Y.COM.TW

WWW.100X.

Figure 10: Amplifier with Split Power Supply


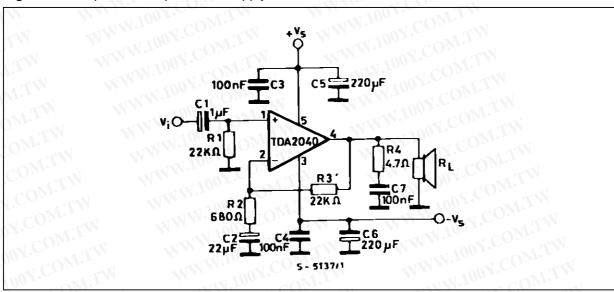


Figure 11: P.C. Board and Components Layout for the Circuit of Figure 10 (1:1 scale)

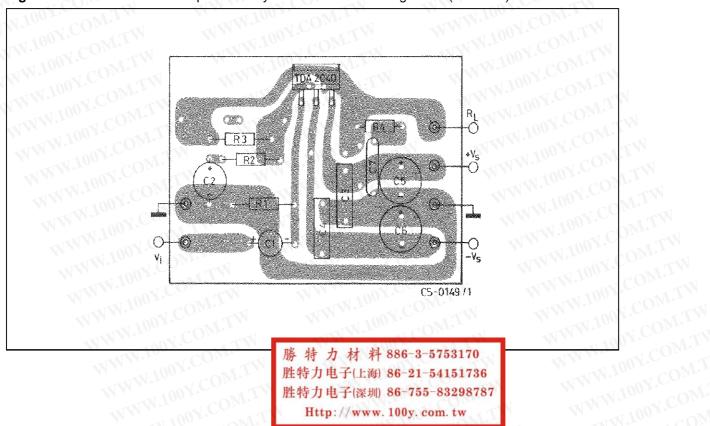

胜特力电子(上海) 86-21-54151736 胜特力电子(深圳) 86-755-83298787 Http://www. 100y. com. tw

WWW.100Y.COM.

Figure 12 : Amplifier with Split Power Supply (see Note)


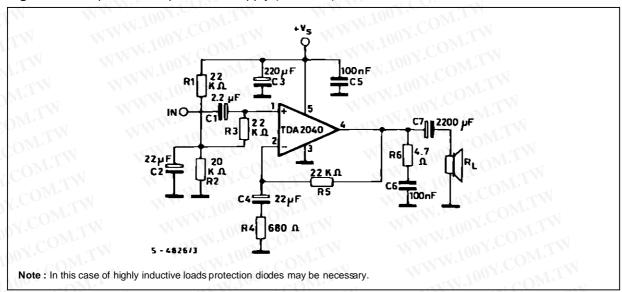


Figure 13: P.C. Board and Components Layout for the Circuit of Figure 12 (1:1 scale)

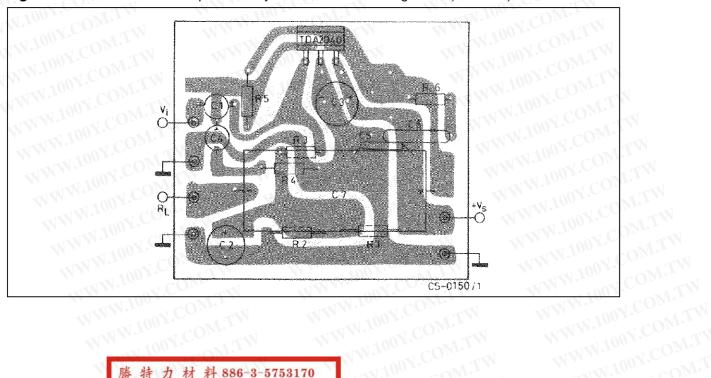

勝 特 力 材 料 886-3-5753170 胜特力电子(上海) 86-21-54151736 胜特力电子(深圳) 86-755-83298787 Http://www.100y.com.tw

WWW.100Y.

WW.100Y.COM.TW

Figure 14: 30W Bridge Amplifier with Split Power Supply


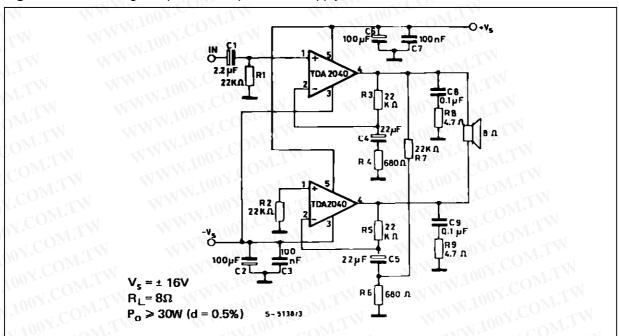


Figure 15: P.C. Board and Components Layout for the Circuit of Figure 14 (1:1 scale)

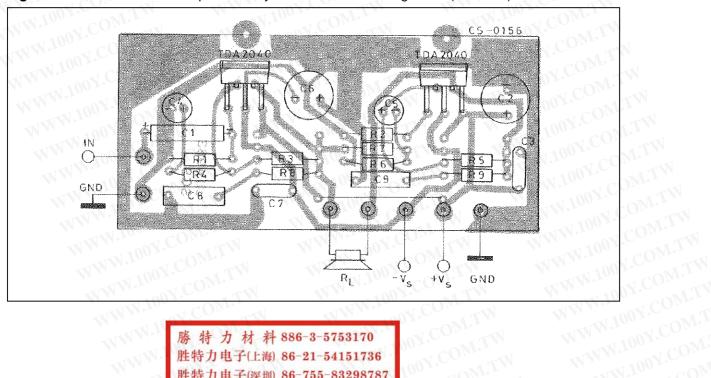

勝 特 力 材 料 886-3-5753170 胜特力电子(上海) 86-21-54151736 胜特力电子(深圳) 86-755-83298787 Http://www.100y.com.tw

8/13

Figure 16: Two Way Hi-Fi System with Active Crossover



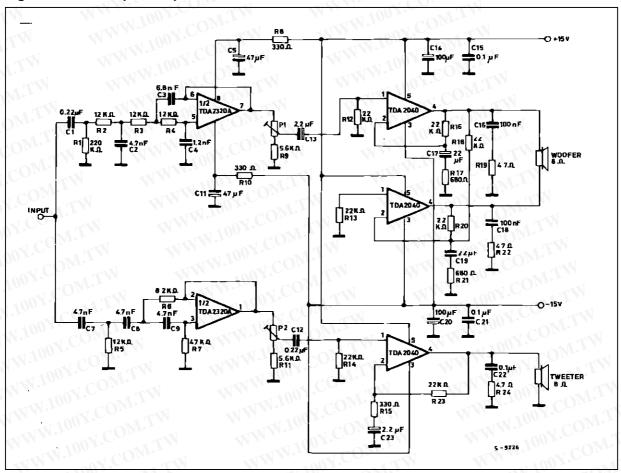


Figure 17: P.C. Board and Components Layout for the Circuit of Figure 16 (1:1 scale)

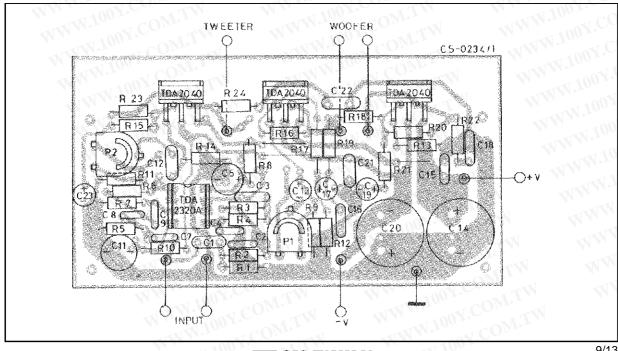

Http://www. 100y. com. tw

Figure 18: Frequency Response

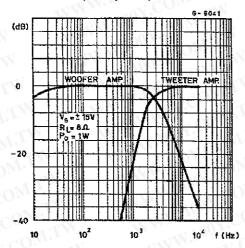

MULTIWAY SPEAKER SYSTEMS AND ACTIVE BOXES

Multiway loudspeaker systems provide the best possible acoustic performance since each loud-speaker is specially designed and optimized to handle a limited range of frequencies. Commonly, these loudspeaker systems divide the audio spectrum into two, three or four bands.


To maintain a flat frequency response over the Hi-Fi audio range the bands covered by each loud-speaker must overlap slightly. Imbalance between the loudspeakers produces unacceptable results therefore it is important to ensure that each unit generates the correct amount of acoustic energy for its segment of the audio spectrum. In this respect it is also important to know the energy distribution of the music spectrum determine the cutoff frequencies of the crossover filters (see Figure 19). As an example, a 100W three-way system with crossover frequencies of 400Hz and 3kHz would require 50W for the woofer, 35W for the midrange unit and 15W for the tweeter.

Both active and passive filters can be used for crossovers but today active filters cost significantly less than a good passive filter using air-cored inductors and non-electrolytic capacitors. In addition, active filters do not suffer from the typical defects of passive filters:

- power loss
- increased impedance seen by the loudspeaker (lower damping)
- difficulty of precise design due to variable loudspeaker impedance

Obviously, active crossovers can only be used if a

Figure 19: Power Distribution versus Frequency

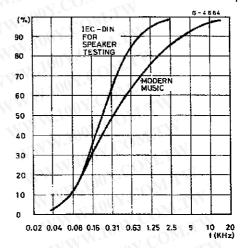


power amplifier is provided for each drive unit. This makes it particularly interesting and economically sound to use monolithic power amplifiers. In some applications, complex filters are not really necessary and simple RC low-pass and high-pass networks (6dB/octave) can be recommended.

The results obtained are excellent because this is the best type of audio filter and the only one free from phase and transient distortion.

The rather poor out of band attenuation of single RC filters means that the loudspeaker must operate linearly well beyond the crossoverfrequency to avoid distortion.

A more effective solution, named "Active Power Filter" by SGS is shown in Figure 20.

Figure 20: Active Power Filter

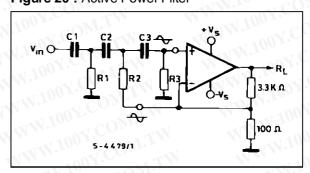

The proposed circuit can realize combined power amplifiers and 12dB/octave or 18dB/octave high-pass or low-pass filters.

In practice, at the input pins of the amplifier two equal and in-phase voltages are available, as required for the active filter operation.

The impedance at the pin (-) is of the order of 100Ω , while that of the pin (+) is very high, which is also what was wanted.

C1 = C2 = C3	R1	R2	R3
22 nF	8.2 kΩ	5.6 kΩ	33 kΩ

The component values calculated for $f_c = 900 Hz$ using a Bessel 3rd order Sallen and Key structure are :

In the block diagram of Figure 21 is represented an active loudspeaker system completely realized using power integrated circuit, rather than the traditional discrete transistors on hybrids, very high quality is obtained by driving the audio spectrum into three bands using active crossovers (TDA2320A) and a separate amplifier and loudspeakers for each band.

A modern subwoofer/midrange/tweeter solution is used.

PRATICAL CONSIDERATION

Printed Circuit Board

The layout shown in Figure 11 should be adopted by the designers. If different layouts are used, the ground points of input 1 and input 2 must be well decoupled from the gorund return of the output in which a high current flows.


Assembly Suggestion

No electrical isolation is needed between the package and the heatsink with single supply voltage configuration.

Application Suggestions

The recommended values of the components are those shown on application circuit of Fig. 10. Different values can be used. The following table can help the designer.

Figure 21: High Power Active Loudspeaker System using TDA2030A and TDA2040

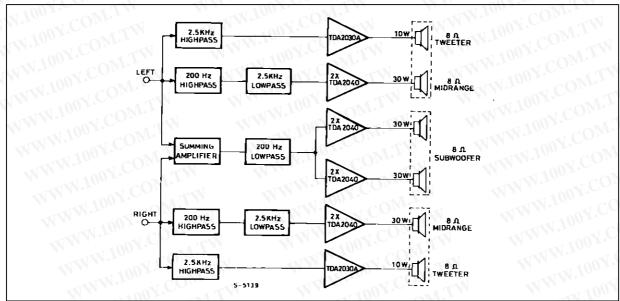

Comp.	Recom. Value	Purpose	Larger than Recommended Value	Smaller than Recommended Value
R1	22kΩ	Non inverting input biasing	Increase of input impedance	Decrease of input impedance
R2	680Ω	Closed loop gain setting	Decrease of gain (*)	Increase of gain
R3	22kΩ	Closed loop gain setting	Increase of gain	Decrease of gain (*)
R4	4.7Ω	Frequency stability	Danger of oscillation at high frequencies with inductive loads	COM. TW WWY
C1	1μF	Input DC decoupling	TINN.	Increase of low frequencies cut-off
C2	22μF	Inverting DC decoupling	1.1 1. 10.	Increase of low frequencies cut-off
C3, C4	0.1μF	Supply voltage bypass	TW WWW	Danger of oscillation
C5, C6	220μF	Supply voltage bypass	M. WANNE	Danger of oscillation
C7	0.1μF	Frequency stability	M. T.	Danger of oscillation

^(*) The value of closed loop gain must be higher than 24dB

Http://www.100y.com.tw

PENTAWATT PACKAGE MECHANICAL DATA

DIM.	mm			inch			
DIWI.	MIN.	TYP.	MAX.	MIN.	TYP.	MAX.	
Α	- 1W.100	COM.	4.8	W.Inc	Mr.	0.189	
C	11/11/100	Y. COLIV	1.37	100 Y.	OM.TW	0.054	
D	2.4	V.COn	2.8	0.094	WT	0.110	
D1	1.2	COMPT	1.35	0.047	COMP	0.053	
TE	0.35	100 X	0.55	0.014		0.022	
F	0.8	ON COM	1.05	0.031	.Co	0.041	
F1	1	Jon	1.4	0.039	COM.	0.055	
G		3.4	CTV	0.126	0.134	0.142	
G1	WW	6.8	W	0.260	0.268	0.276	
H2		W.Jus	10.4		COM	0.409	
H3	10.05	TI 100 Y.	10.4	0.396	00.7	0.409	
COL	W W	17.85	O" TW	MM.	0.703		
L1	.=1	15.75	COMP		0.620		
L2		21.4	-oM.T.V	-11	0.843	V. I.	
L3	TW .	22.5	CO	WW	0.886	WILL	
L5	2.6	TANN. TO	3	0.102	M. T. C.C.	0.118	
L6	15.1	100	15.8	0.594	W.100	0.622	
L7.CO	6	MAL	6.6	0.236	11007.0	0.260	
M	Mr.	4.5	COM	- XX	0.177	COM	
M1	MITW	4	00_{1} . 00_{M} .	1	0.157	COM	
Dia	3.65	M. W.	3.85	0.144	1 1 1003	0.152	

